

Timothy Ho, Chuizheng Kong, Shengyi Shen

LITEC

Section 3

Group Member 1 Pseudocode

compiler directives

```
#include <c8051_SDCC.h>
```

```
#include <stdio.h>
```

declare global variables

```
sbit PB1, PB2, SS, LED0, BILED0, BILED1, BUZZER
```

function prototypes

```
void Port_Init(void)
```

```
void Set_Outputs(void)
```

main function

declare local variables

(NONE)

initialization functions

```
Sys_Init();
```

```
putchar(' ');
```

```
Port_Init();
```

Begin infinite loop

execute Set_Outputs(void) function to read sbit inputs and set sbit
outputs

End infinite loop

End main function

Functions

```
void Port_Init(void)
```

```
    Set SFRs P2, P3, P2MDOUT & P3MDOUT so P2.0, P3.0 & P3.1 are inputs,  
    P3.3, P3.4, P3.6 & P3.7 are outputs
```

```
End Port_Init
```

```
void Set_Outputs(void)
```

```
    If SS is off then
```

```
        LED0 is on, BILED0 is off, BILED1 is off, BUZZER is off
```

```
        Print "Slide Switch is OFF"
```

```
    Else (this means SS is on)
```

```
        Print "Slide Switch is ON and LED0 is off"
```

```
        If (PB1 is pushed and PB2 is pushed) then
```

```
            BILED0 is off, BILED1 is off, BUZZER is on
```

```
            Print "Pushbutton 1 and 2 ACTIVATED"
```

```
        Else if (PB1 is pushed and PB2 is released) then
```

```
            BILED0 is Green, BILED1 is off, BUZZER is off
```

```
            Print "Pushbutton 1 ACTIVATED"
```

```
        Else if (PB1 is released and PB2 is pushed) then
```

```
            BILED0 is off, BILED1 is Red, BUZZER is off
```

```
            Print "Pushbutton 2 ACTIVATED"
```

```
        Else BILED0 is off, BILED1 is off, BUZZER is off
```

```
End Set_Outputs
```

EVB Pin

Port Bit

Bit Addresses & Labels

Software Initializations

1	2
3	4
5	6
7	8
9	10
11	12
13	14
15	16
17	18
19	20
21	22
23	24
25	26
27	28
29	30
31	32
33	34
35	36
37	38
39	40
41	60

1.		
2.		
3.		
4.		
5.		
6.		
7.		
8.		
9.		
10.		
11.		
12.		
13.		
14.		
15.		
16.		
17.		
18.		
19.		
20.		
21.		
22.		
23.		
24.		
25.		
26.		
27.		
28.		
29.	P2.0	0xA0 Slide Switch
30.		
31.	P3.6	0xB6 LED0
32.	P3.7	0xB7 Buzzer
33.	P3.4	0xB4 BILED
34.		
35.		
36.	P3.3	0xB3 BILED
37.	P3.1	0xB1 PB2
38.	P3.0	0xB0 PB1
39.		
40.		

A) Port I/O

P3MDOUT &= ~0x03;
P3MDOUT = 0xD8;
P3 = 0x03;
P2MDOUT &= ~0x01;
P2 = 0x01;

B) Timers

C) Interrupts

D) A/D

E) PCA

F) XBAR

G) I2C

Laboratory Worksheet #01

Number Systems Exercise

Convert the following decimal numbers to binary:

- | | | |
|----|-----|----------------|
| 1) | 14 | 0000 1110 |
| 2) | 189 | 1011 1101 |
| 3) | 257 | 0001 0000 0001 |
| 4) | 472 | 0001 1101 1000 |

Convert the following decimal numbers to hex:

- | | | |
|----|-----|-------|
| 5) | 14 | 0x0E |
| 6) | 189 | 0xBD |
| 7) | 257 | 0x101 |
| 8) | 472 | 0x1D8 |

Convert the following hex numbers to decimal:

- | | | |
|-----|--------|-------|
| 9) | 0x37 | 55 |
| 10) | 0xAB | 171 |
| 11) | 0x0147 | 327 |
| 12) | 0x2AE1 | 10977 |

Convert the following hex numbers to binary:

- | | | |
|-----|--------|---------------------|
| 13) | 0x37 | 0011 0111 |
| 14) | 0xAB | 1010 1011 |
| 15) | 0x0147 | 0000 0001 0100 0111 |
| 16) | 0x2AE1 | 0010 0110 1110 0001 |

Convert the following binary numbers to hex:

- | | | |
|-----|---------------------|--------|
| 17) | 0010 1101 | 0x2B |
| 18) | 1010 1010 | 0xAA |
| 19) | 1110 0011 | 0xE3 |
| 20) | 0010 1001 1011 0101 | 0x29B5 |

Convert the following binary numbers to decimal:

- | | | |
|-----|---------------------|-------|
| 21) | 0010 1101 | 45 |
| 22) | 1010 1010 | 170 |
| 23) | 1110 0011 | 227 |
| 24) | 0010 1001 1011 0101 | 10677 |

When complete, include Worksheet 1 with your Laboratory 1-1 Pre-lab submission.

Laboratory Worksheet #02

Logic Exercise

Answer the following questions given:

```
char a,b,c,d;
```

```
a = 0x00;
```

```
b = 0x0F;
```

```
c = 0x09;
```

What is the value of **d** after execution of the following lines?

1) **d = a & c;**

0x00

2) **d = b & c;**

0x09

3) **d = b & 0x04;**

0x04

4) **d = b & 0x33;**

0x03

5) **d = b & !c;**

0x00

Are the following TRUE or FALSE?

6) **(a && c)**

False

7) **(b && c)**

True

8) **(b && 0x04)**

True

What is the value of **d** after execution of the following lines?

9) **d = a | c;**

0x09

10) **d = b | 0x10;**

0x1F

11) **d = b | a;**

0x07

12) **d = b | !a;**

0x0F

Convert the following hex numbers to binary:

13) **(a || c)**

True

14) **(a || (c & 0x10))**

False

15) **(a || !b)**

False

When complete, include Worksheet 2 with your Laboratory 1-1 Pre-lab submission.

Laboratory Worksheet #03

Hardware: Digital Input and Output Exercise

When developing hardware circuits, it is recommended to build and test small circuits that will later be expanded upon. This first project involves the use of a couple key components (74365 chips, LEDs, BILEDs, Buzzers, Resistors) that play an important role in both digital input and output.

Construct the circuit shown below. Debugging the hardware circuit is performed using the Logic Probe available in the Toolbox. Directions on using the logic probe can be found not only in the LITEC Multimedia Tutorials, but also in Chapter 2 of your lab manual. Also, please refer to Appendix B, Figure B.1 in the lab manual concerning the connections of **+5V** and **Ground** on the Smart Car connection board.

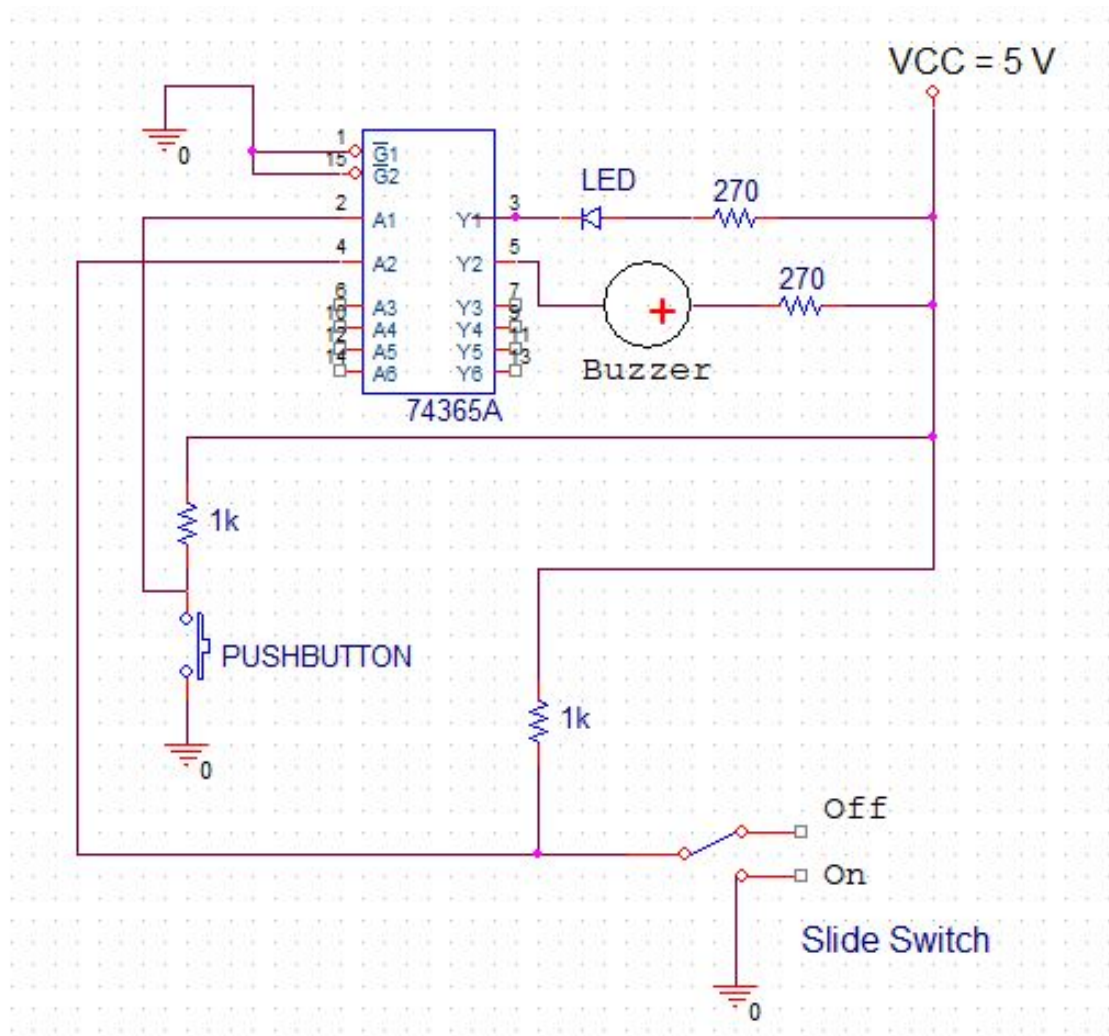


Figure 1: Worksheet 3 Schematic

Note: In the above circuit schematic, the power connections for the 74365 chip are not shown. This format is common to circuit schematics, where the implementer is expected to know the connections for power and ground.

1) Using the on-line data sheets, determine all pins of the 74F365 that need to be connected to a high voltage (VCC or +5V) and those that need to be connected to a low voltage (GND or 0V).

2) Using the Logic Probe, what value (high/low) do you get when you test pin #16 on the 74F365 buffer? What color is Logic Probe LED?

3) What about when you test pin #1 on the same chip?

4) What voltage values are the buffer gate outputs connected to the LED and Buzzer (pin 3 and pin 5 of the Hex buffer, respectively) when the slide switch is ON and the button is pushed? Are the LED and Buzzer on (lit/noisy) or off (unlit/no sound)?

5) Connect pins 1 and 15 to power (5V) instead of ground. What happens when you push the button or move the slide switch?

6) Disconnect pins 1 and 15 completely (so they are not connected to anything). The pins are now considered 'floating', which means their voltage level is uncertain. What happens when you push the button or move the slide switch?

When complete, include Worksheet 3 with your Laboratory 1-1 Pre-lab submission.

Laboratory Worksheet #04

Hardware: Digital Input and Output Exercise

When complete, insert Worksheet 04 in your laboratory notebook. Worksheets are required when the notebooks are graded. Perform any necessary calculations on the left page of the notebook where the worksheet is placed. Keep individual copies of the worksheet for your own records. This worksheet is a pre-lab exercise to be done before starting Lab 1-1 and should not be confused with the lab.

One of the important aspects of the software is initializing Special Function Registers (SFRs). In Laboratory 1, you will create initialization functions for Port I/O, which involves setting the correct SFR bits to 0 or 1, as needed. The logic assignment operations developed in Worksheet 2 are used to set the appropriate bits without changing the other bits.

Additionally, using the `sbit` command to assign a variable name to a single bit in the SFR can make programming and code execution much simpler. You will read from or write to individual bits when performing Input/Output operations on the Port pins. These read and write operations will be performed using the `sbit` labels assigned to the specific Port pins.

As an example problem, Port 2 will be configured for both input and output. Note, this is an example problem and is not to confused with Laboratory 1. The followed Port bits will be assigned as inputs or outputs:

$Pn.m$ (Port n , bit m)	Description	Bit Label
P2.1	Input bit for doorbell	DB
P2.3	Input bit for an alarm clock	AC
P2.5	Output bit for a porch light	Porch
P2.6	Input bit for a garage door	GD

All other bits are considered previously assigned and should not be changed.

Refer to the manual section *Input/Output Ports on the C8051* or the course slides to determine the syntax. The memory locations for Port 2 bit 0 is 0xA0, Port 2 bit 1 is 0xA1, through Port 2 bit 7 at 0xA7. Complete the following four lines of code to assign the labels to the appropriate bit using the `sbit` command.

```
sbit at 0xA1 DB; // remember to include the double "_"
__sbit __at 0xA3 AC;
__sbit __at 0xA5 Porch;
__sbit __at 0xA6 GD;
```


In the following SFR data tables, indicate whether the bit should be set high (1), low (0), or undetermined/unchanged (X).

P2MDOUT (input bits are set to 0, output bits are set to 1, unchanged bits are indicated with an X)

bit	7	6	5	4	3	2	1	0
	x	0	1	x	0	x	0	x

Determine the bit mask for setting the appropriate bits high (logic 1) P2MDOUT | = 0x20 ;

Determine the bit mask for setting the appropriate bits low (logic 0) P2MDOUT & = ~0x4A ;

P2 (input bits are set to 1 which is a high impedance state, all other bits are unchanged X)

bit	7	6	5	4	3	2	1	0
	x	1	x	x	1	x	1	x

Determine the bit mask for setting the appropriate bits high (logic 1) P2 | = 0x4A ;

In summary, using the above definitions, complete the Port_Init() function for this example.

```

Port_Init()
{
    P2MDOUT &= ~0x4A ;           //configure Port 2 bits as inputs
    P2MDOUT |= 0x20 ;           //configure Port 2 bits as outputs
    P2 |= 0x4A ;           //set Port 2 input bits to a high impedance state
}

```

When complete, include Worksheet 4 with your Laboratory 1-1 Pre-lab submission.